



# OCR A Level Computer Science



Your notes

## 4.3 Boolean Algebra

### Contents

- \* Boolean Logic
- \* Karnaugh Maps
- \* Simplifying Boolean Algebra
- \* Flip Flop Circuits
- \* Adder Circuits



Your notes

## Boolean Logic

# Logic Gates

## What is Boolean Logic?

- Boolean logic is used in computer science and electronics to make **logical decisions**
- Boolean operators are either **TRUE** or **FALSE**, often represented as **1** or **0**
- Inputs and outputs are given **letters to represent them**
- To define Boolean logic we use **special symbols** to make **writing expressions** much **easier**

## Combination of Boolean operators

- Can be **combined** to form more **complex** expressions
- Use **parentheses** to clarify the **order** of operations  
**Example:** NOT (TRUE AND FALSE) = TRUE

## Evaluating Boolean expressions

- There is a specific sequence for evaluating expressions with **multiple operators** just like in normal maths where **BIDMAS** applies
- **Brackets come first** then **NOT** then **AND** then **OR**
- Using Brackets can **alter the standard order** of operations
- Expressions within **parentheses** are **evaluated first**, following the same **NOT, AND, OR** precedence inside the parentheses
- **Example:** NOT (TRUE AND FALSE) equals NOT FALSE, which equals TRUE


## Logic Gates

- Logic gates are a visual way of representing a Boolean expression
- The logic gates covered in this course are:
  - **Conjunction (AND)**
  - **Disjunction (OR)**
  - **Negation (NOT)**
  - **Exclusive disjunction (XOR)**




Your notes


## Conjunction (AND)

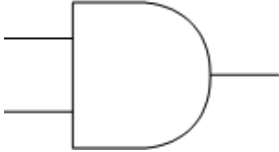Operation	Circuit symbol	Notes
$A \wedge B$ $A \cdot B$		Returns TRUE only if <b>both</b> inputs are TRUE  <b>TRUE AND TRUE = TRUE</b>  Otherwise = FALSE  Next <b>highest precedence</b> after NOT  <b>Executes before OR operations</b>

## Disjunction (OR)

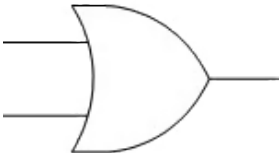Operation	Circuit symbol	Explanation
$A \vee B$ $A + B$		Returns TRUE if <b>either</b> input is TRUE  <b>TRUE OR FALSE = TRUE</b>  <b>FALSE OR FALSE = FALSE</b>  <b>Lowest precedence</b> in Boolean expressions  Executes <b>after NOT and AND</b> operations


## Negation (NOT)

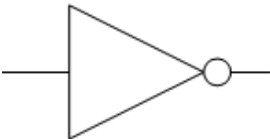Symbol	Circuit symbol	Notes
$\neg A$ $\overline{A}$		<b>Inverts</b> the input value  NOT TRUE = FALSE  NOT FALSE = TRUE  <b>Highest precedence</b> in Boolean expressions  Executes <b>before AND and OR</b> operations

## Exclusive Disjunction (XOR)



Your notes

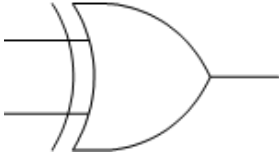Operation	Circuit symbol	Notes
$A \nabla B$ $A$ $\oplus$ $B$		<p>Outputs <b>TRUE</b> if the <b>inputs are different</b></p> <p>Outputs <b>FALSE</b> if <b>they are the same</b></p>




### Examiner Tip

- Understanding the order of operations is crucial for correctly interpreting complex Boolean expressions
- Misunderstanding the order can lead to incorrect results
- Always use parentheses for clarity when combining multiple Boolean operations

## Truth Tables

- A tool used in logic and computer science to **visualise** the **results** of **Boolean expressions**
- They represent **all possible inputs** and the **associated outputs** for a **given Boolean expression**

## Conjunction (AND)

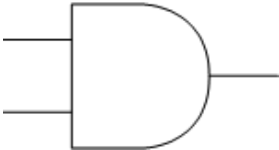
Circuit symbol	Truth Table									
	<table><tr><th>A</th><th>B</th><th>A ^ B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr></table>	A	B	A ^ B	0	0	0	0	1	0
A	B	A ^ B								
0	0	0								
0	1	0								




Your notes

	1	0	0
	1	1	1

## Disjunction (OR)

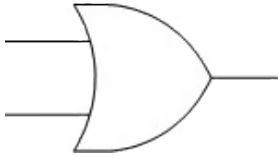Circuit symbol	Truth Table															
	<table><tr><th>A</th><th>B</th><th><math>A \vee B</math></th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	$A \vee B$	0	0	0	0	1	1	1	0	1	1	1	1
A	B	$A \vee B$														
0	0	0														
0	1	1														
1	0	1														
1	1	1														


## Negation (NOT)

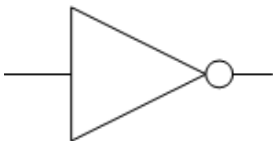Circuit symbol	Truth Table						
	<table> <tr> <th>A</th><th><math>\neg A</math></th></tr> <tr> <td>0</td><td>1</td></tr> <tr> <td>1</td><td>0</td></tr> </table>	A	$\neg A$	0	1	1	0
A	$\neg A$						
0	1						
1	0						

## Exclusive Disjunction (XOR)




Your notes

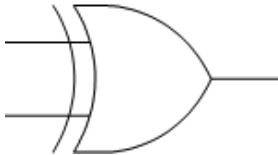Circuit symbol	Truth Table															
	<table><tr><th>A</th><th>B</th><th><math>A \vee B</math></th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	$A \vee B$	0	0	0	0	1	1	1	0	1	1	1	0
A	B	$A \vee B$														
0	0	0														
0	1	1														
1	0	1														
1	1	0														


 
### Worked Example

Daniel is an engineer. He has created the following logic circuit as shown



Complete the truth table below for the logic circuit shown

A	B	C	D	X
---	---	---	---	---



Your notes

0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

4 marks

Answer:

Example answer that gets full marks:

A	B	C	Calculating D	D	Calculating X	X	Mark
0	0	0	D is the result of A <u>AND</u> B	0	X is the result of D <u>XOR</u> C	0	1 Mark
0	0	1		0		1	
0	1	0		0		0	1 Mark
0	1	1		0		1	
1	0	0		0		0	1 Mark
1	0	1		0		1	
1	1	0		1		1	1 Mark
1	1	1		1		0	



Your notes

## Karnaugh Maps

# Karnaugh Maps

## What is a Karnaugh Map?

- This is a tool that is used for **simplifying Boolean algebra expressions**
- It offers a **visual method** of **grouping together expressions** with **common factors**
- The format of the map makes it **easy to identify** and **eliminate redundant terms**
- They are used in digital logic design, such as simplifying the logic of digital circuits

## Steps:

1. **Create the Map:** Each cell in the grid corresponds to a term in the Boolean expression. Fill cells with 1s and 0s corresponding to the output of that term
2. **Grouping:** Group the 1s in the grid. Each group must be a rectangle and the size of the group must be a power of 2. A cell can be part of multiple groups
3. **Simplifying:** Write down a simplified Boolean expression for each group. The simplified expression for a group consists of the variables that remain constant in all terms in the group
4. **Final Expression:** Combine the simplified expressions from each group using OR operations to get the final simplified Boolean expression

## Creating Karnaugh Maps

- A Karnaugh Map (**KMap**) can be used to **simplify a Boolean expression** with 2 inputs
- Here is an example for the expression  **$A \vee B$  ( $A \text{ OR } B$ )**

## Step 1

- **Add each variable** starting with **A** at the top and **B** down the side
- **Add each possible state** for **A** and **B**





Your notes

		A	A
		0	1
B	0		
B	1		

## Step 2

- Take each expression in turn **separated** by the V (OR)
- First look at **A** on it's own
- Find **all cells where A is 1**
- Add 1 to the cell**

		A	A
		0	1
B	0		1
B	1		1

## Step 3

- Repeat for B



Your notes

		A	A
		0	1
B	0		1
B	1	1	1

## Step 4

- This is now a **completed KMap** for the expression  $A \vee B$  ( $A \text{ OR } B$ )

		A	A
		0	1
B	0		1
B	1	1	1

## Simplifying Expressions Using Karnaugh Maps

Simplify  $\neg A \wedge \neg B \wedge C \vee \neg A \wedge B \wedge \neg C \vee A \wedge \neg B \wedge C \vee A \wedge B$  using a KMap.

In this example there will be **3 variables** A, B and C so the empty KMap will look like this:



Your notes

		AB			
		00	01	11	10
C	0				
	1				

## Step 1:

Split this long term at each **OR** giving 4 smaller expressions (subterms) to add to the table:

- $\neg A \neg B^C$
- $\neg A^B \neg C$
- $A^B^C$
- $A^B$

## Step 2:

- Take the first subterm  $\neg A^B^C$
- Put a **1** in the map for **every cell where this term would be TRUE (1)**
- So if **A** and **B** were **0** and **C** was **1** this subterm would be 1
- So put a **1** in every cell in the KMap where **A is 0, B is 0** and **C is 1**

		AB			
		00	01	11	10
C	0				
	1	1			

## Step 3:

- The next subterm is  $\neg A^B \neg C$
- Put a **1** in the KMap where **A is 0, B is 1** and **C is 0**



Your notes

		AB			
		00	01	11	10
C	0		1		
	1	1			

## Step 4:

- The next subterm is  $A \neg B \wedge C$
- Put a 1 in the KMap where **A is 1**, **B is 0** and **C is 1**

		AB			
		00	01	11	10
C	0		1		
	1	1			1

## Step 5:

- The final subterm is  $A \wedge B$
- Put a 1 in the KMap where **A is 1** and **B is 1** (2 cells this time)

		AB			
		00	01	11	10
C	0		1	1	
	1	1		1	1

## Making the groups



Your notes

- Once you have written the 1s and 0s into your KMap, you can then use this to **simply the expression**
- In order to do this, you need to **identify the groups**
- This is the **key** to using the Karnaugh map to derive the simplified expression
- The aim of making the groups is to
  - Make rectangular groups**
  - Make groups that are as large as possible**
  - Make groups that contain either 8, 4, 2 or 1 ones**
  - Groups can overlap** (i.e. some ones can be in multiple groups)
  - The Karnaugh map 'grid' wraps round in all directions so the groups can wrap round**

## Example grouping

**Group 1:**

So this would be one group.

		AB			
		00	01	11	10
C	0	1		1	1
	1	1		1	1

This group would represent **A** since within this group both C and B change (have zeros and ones) whereas for A all the cells are one.

**Group 2:**

This would be another group (**note the wrapping around**).



Your notes

		AB			
		00	01	11	10
C	0	1		1	1
	1	1		1	1

This group would represent  $\neg B$  since within this group both A and C change (have zeros and ones) whereas for B all the cells are zero

#### Final simplified expression

- To get the final simplified expression we **OR** the terms representing the two groups together.
- So the simplified expression is  $A \vee \neg B$



#### Examiner Tip

In questions where you have to use a Karnaugh Map always show the groups by drawing a box/circle round them.



#### Worked Example

A Boolean expression is entered into a Karnaugh map.



Your notes


		AB			
		00	01	11	10
CD	00	1	1	1	1
	01	1	1	1	1
	11	0	1	1	0
	10	0	1	1	0

Give a simplified version of the expression using the Karnaugh map.

You must show your working

3 marks

How to answer this question:

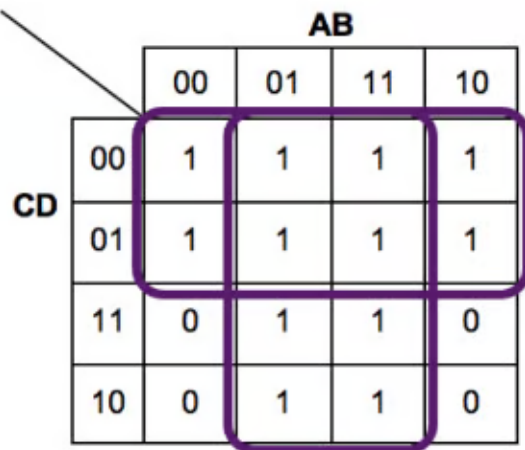

		AB			
		00	01	11	10
CD	00	1	1	1	1
	01	1	1	1	1
	11	0	1	1	0
	10	0	1	1	0

- Looking at the group of 8 in the middle of the map, for all the cells in the group the variable B is always a 1
  - The 3 other variables change across the group (i.e. for some cells they are 0 and for others they are 1)
- So this group is B

- Looking at the other group of 8, for all the cells in this group, C is always 0 but the other 3 variables can be 1 or 0 in this group So this group simplifies to  $\neg C$

Answer:

**Answer that gets full marks:**

$B \vee \neg C$



Your notes





Your notes

## Simplifying Boolean Algebra

### De Morgan's Law

- **Complex expressions** can be made **simpler** using the rules of **Boolean algebra**
- This is a **more powerful simplification** method than Karnaugh maps and can simplify expressions that Karnaugh maps cannot
- There are various different **rules** that you need to learn and that can then be applied to certain expressions to simplify them
- **Combining these rules** can mean that **complex expressions** can be **reduced to much simpler ones**

### General rules

#### General AND rules

- $X \text{ AND } 0 = 0$
- $X \text{ AND } 1 = X$
- $X \text{ AND } A = X$
- $\text{NOT } X \text{ AND } X = 0$

Note, the value of  $X$  is unknown and it is used as a placeholder. Therefore  $X \text{ AND } 1 = X$  means that the output will be whatever the value of  $X$  is.

#### General OR rules

- $X \text{ OR } 0 = X$   
 $X \text{ OR } 1 = 1$   
 $X \text{ OR } A = X$   
 $\text{NOT } X \text{ OR } X = 1$

### DeMorgan's Law

- This provides a strategy for simplifying expressions that include a negation of a conjunction or disjunction (simplifying by inverting all variable)
- **NOT(A AND B)** is the same as **(NOT A) OR (NOT B)**



Your notes

NOT (A AND B)			$\neg(A \wedge B)$	is the same as	(NOT A) OR (NOT B)				$\neg A \vee \neg B$
A	B	A AND B	NOT (A AND B)		A	B	NOT A	NOT B	(NOT A) OR (NOT B)
0	0	0	1	$\equiv$	0	0	1	1	1
0	1	0	1		0	1	1	0	1
1	0	0	1		1	0	0	1	1
1	1	1	0		1	1	0	0	0

- **Step 1**
  - Change AND to OR (or vice versa) -  $\neg(A \vee B)$
- **Step 2**
  - NOT the terms either side of the operator -  $\neg(\neg A \vee \neg B)$
- **Step 3**
  - NOT everything that has changed -  $\neg\neg(\neg A \vee \neg B)$
- **Step 4**
  - Get rid of any double negation -  $(\neg A \vee \neg B)$
- **Step 5**
  - Remove any unnecessary brackets -  $\neg A \vee \neg B$
- **NOT(A OR B) is the same as (NOT A) AND (NOT B)**

NOT (A OR B)			$\neg(A \vee B)$	is the same as	(NOT A) AND (NOT B)				$\neg A \wedge \neg B$
A	B	A OR B	NOT (A OR B)		A	B	NOT A	NOT B	(NOT A) AND (NOT B)
0	0	0	1	$\equiv$	0	0	1	1	1
0	1	1	0		0	1	1	0	0
1	0	1	0		1	0	0	1	0
1	1	1	0		1	1	0	0	0

- **Step 1**
  - Change AND to OR (or vice versa) -  $\neg(A \wedge B)$



Your notes

**Step 2**

- NOT the terms either side of the operator -  $\neg(\neg A \wedge \neg B)$

**Step 3**

- NOT everything that has changed -  $\neg\neg(\neg A \wedge \neg B)$

**Step 4**

- Get rid of any double negation -  $(\neg A \wedge \neg B)$

**Step 5**

- Remove any unnecessary brackets -  $\neg A \wedge \neg B$
- Simplifying using this law allows the use of **only NAND or NOR gates** which makes **building microprocessors** much **easier** (i.e. Flash drives)

## Distribution

### Distributive Law

- This explains how AND and OR interact with each other
- This is a bit like factorising in normal maths
- **A AND (B OR C)** is the same as **(A AND B) OR (A AND C)**
- **A OR (B AND C)** is the same as **(A OR B) AND (A OR C)**

**Real-life example**

- "You can pick one subject from group A and either one from group B or group C"
- is the same as
- "You can pick one subject from group A and one from group B or one subject from group A and one from group C"

## Association

### Associative Law

- This explains how variables associate in expressions of more than two variables
- Allows us to remove brackets and regroup variables
- **(A AND B) AND C** is the same as **A AND (B AND C)** is the same as **A AND B AND C**
- **(A OR B) OR C** is the same as **A OR (B OR C)** is the same as **A OR B OR C**



Your notes

**Real-life example**

- *"Zameen and her friends, Zahra and Ella have been chosen to represent the school"*
- is the same as
- *"Zameen and Zahra, and their friend Ella have been chosen to represent the school"*
- is the same as
- *"Zameen, Zahra and Ella have been chosen to the represent the school"*

## Commutation

### Commutative Law

- States that the order of the variables does not change the truth value of the expression
- **A AND B** is the same as **B AND A**
- **A OR B** is the same as **B OR A**

**Real-life example**

- *"Fynn and George won gold medals"*
- is the same as
- *George and Fynn won gold medals"*

## Double Negation

### Double Negation Law

- States that the double negation of a variable results in the original variable
- $\text{NOT}(\text{NOT}(A)) = A$

**Real-life example**

- *"I don't not want to visit the castle"*
- is the same as
- *"I do want to visit the castle"*

**Worked Example**



Your notes

## SIMPLIFYING EXPRESSION EXAMPLE

Simplify  $(A \vee B) \wedge (A \vee C)$

How to answer this question:

### Step one – Distribution

This is a bit like multiplying out the brackets in an expression in regular maths. Think of OR being like ADD and AND being like MULTIPLY.

$$(A \vee B) \wedge (A \vee C)$$

becomes

$$(A \wedge A) \vee (B \wedge A) \vee (A \wedge C) \vee (B \wedge C)$$

### Step two – General rules

Since  $(A \wedge A)$  is just  $A$  we can replace this term in the expression with a simpler one.

$$(A \wedge A) \vee (B \wedge A) \vee (A \wedge C) \vee (B \wedge C)$$

becomes

$$A \vee (B \wedge A) \vee (A \wedge C) \vee (B \wedge C)$$

### Step three – Commutation

This means the order of the logical operators does not matter so can change  $(B \wedge A)$  into  $(A \wedge B)$ .

$$A \vee (B \wedge A) \vee (A \wedge C) \vee (B \wedge C)$$

becomes

$$A \vee (A \wedge B) \vee (A \wedge C) \vee (B \wedge C)$$

### Step four – Absorption

This rule says that  $A \text{ AND } (A \text{ OR } B) = A$ .

$$A \vee (A \wedge B) \vee (A \wedge C) \vee (B \wedge C)$$

becomes

$$A \vee (A \wedge C) \vee (B \wedge C)$$

### Step five – Another absorption

Again this rule says that  $A \text{ AND } (A \text{ OR } C) = A$  so

$$A \vee (A \wedge C) \vee (B \wedge C)$$

becomes

$$A \vee (B \wedge C)$$

Example answer that gets full marks:

$$A \vee (B \wedge C)$$



Your notes

## Flip Flop Circuits

# D Type Flip Flops

## What is a D Type Flip Flop?


- A **fundamental component** in **digital circuits** and **computer memory**
- Can be referred to as **Positive Edge Triggered**

## Key Features

- Contains **two stable states**, making it a type of **bistable circuit**
- Used to **store the state of 1 bit of data**
- Changes state on the **edge of the clock pulse**
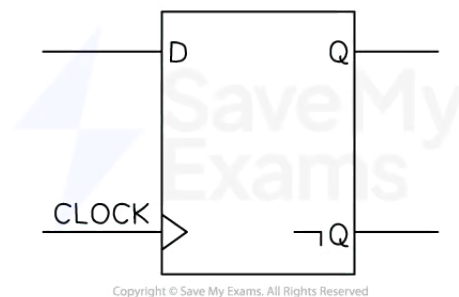
## Components

- Data input (**D**)
- Clock input (**CLK**)
- Two outputs: **Q** and **NOT(Q)**



## D Type Flip Flop Components

## Operation

- On the rising edge of the clock pulse:
  - If D is **high (1)**, Q goes **high** and NOT(Q) goes **low**
  - If D is **low (0)**, Q goes **low** and NOT(Q) goes **high**

- The state of Q holds or "**remembers**" its value until the **next** rising clock edge

## Use Cases

- Forms the basis of most types of flip flops and latches
- Used in **shift registers**, **counters**, and **memory units**
- Helpful in **edge-triggered devices**, **synchronous circuits**, and **data storage**




Your notes


 
### Examiner Tip

You will not be asked to recall the logic gates that make up a D-type flip flop and they can be made from various different gates

They are often built using NAND gates which are AND gates that have their output inverted:



D Type Flip Flop Logic Gates




### Worked Example

- Draw the output of the Flip Flop on the diagram below




Your notes

 

Copyright © Save My Exams. All Rights Reserved
 
### D Type Flip Flop Question

- For a question like this remember that the output line Q that you are asked to draw wants to be the same as the input D BUT it can only change when the clock signal changes from low to high (i.e. at the dotted lines)
- At the start assume Q starts the same as D (low in this case)
- Then draw it along from left to right until you get to a vertical dotted line (in an exam you would draw these lines on to help you if they weren't there)
- At each dotted line, Q has the chance to change to whatever D is



Copyright © Save My Exams. All Rights Reserved


### D Type Flip Flop Working 1

- So at the first line, D is low so Q stays low
- At the second dotted line D has changed to high so now Q can become high






Your notes

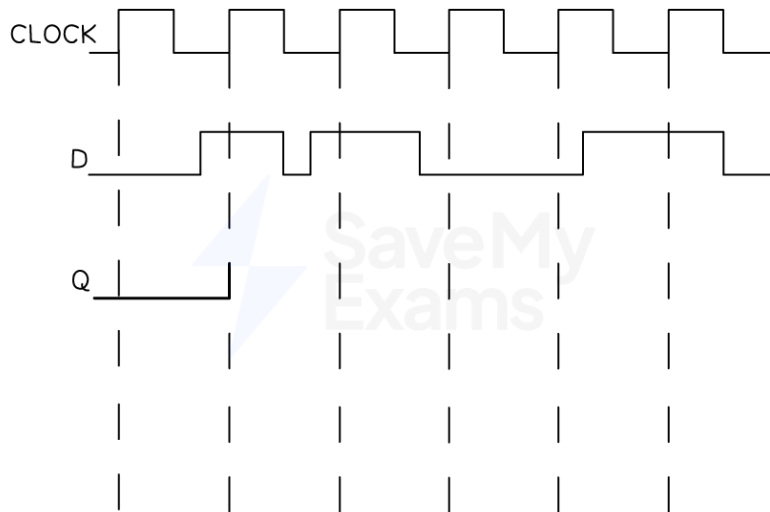

Copyright © Save My Exams. All Rights Reserved
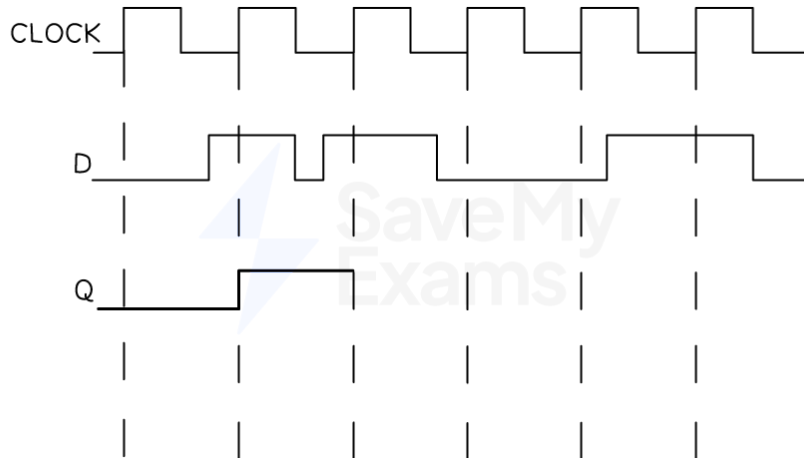
### D Type Flip Flop Working 2

- Q now stays high until the next rising edge of the clock (the next dotted line) where it gets another chance to change, but here D is still high so Q stays high




Copyright © Save My Exams. All Rights Reserved

### D Type Flip Flop Working 3

- And you continue to do this until you reach the right hand side of the diagram



Your notes

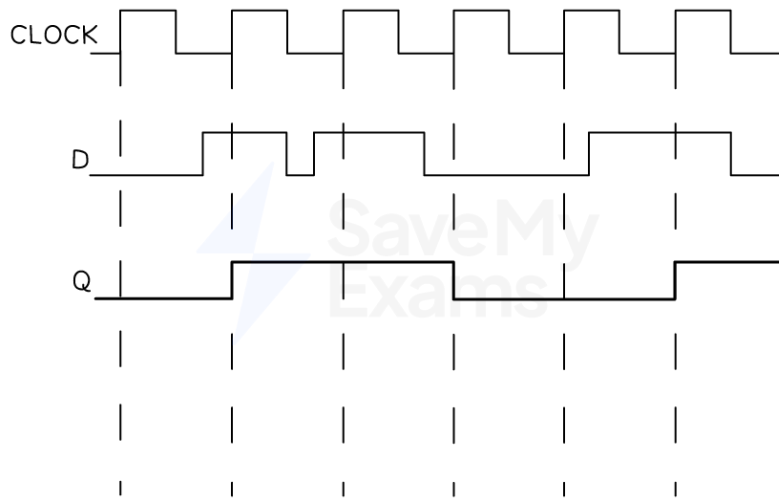

D Type Flip Flop Working 4



Your notes

## Adder Circuits

### Half Adders

#### What is a Half Adder Circuit?

- Basic digital circuit used in computation to perform the **addition** of **two single bit numbers**.
- Has **two inputs**, usually labelled as **A** and **B**
- Produces **two outputs** labelled **Carry out** ( $C_{out}$ ) and **Sum**(s)

A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
		A AND B	A XOR B

- Remember that you are **adding together** the **binary numbers** represented by **A** and **B**
- Create the  **$C_{out}$  column first** then for each row you can just **add A and B together** and write the **answer in 2 bits** in the  **$C_{out}$**  and **S** columns
  - For example in row 2, A is 0 and B is 1 and  $0+1=1$ , which is 01 in 2 bits ( $C_{out}$  0 and Sum 1)
  - In the last row, A is 1 and B is 1 and  $1+1=2$  which is 10 in 2 bit binary ( $C_{out}$  1 and Sum 0)

#### Drawing a Half Adder Circuit

- A half adder circuit has **two inputs**, typically labelled as **A** and **B**, and **two outputs**: the **Sum** (S) and **Carry** ( $C_{out}$ ). This circuit can be created using an **XOR gate** for the **Sum output** and an **AND gate** for the **Carry output**
- Label Inputs:**
  - Begin by drawing two lines on the left side of your paper or drawing space. Label the top line as '**A**' and the bottom line as '**B**'. These represent your **inputs**




Your notes

▪ **XOR Gate (Sum):**

- **Draw an XOR gate** (often a shape like a curved 'D' or a shape similar to an OR gate but with an additional curved line on the input side) in the middle of the paper or drawing space. Connect the A and B lines to the two inputs of the **XOR gate**
- The output from the XOR gate is the '**Sum**'. Draw a line from the output of the **XOR gate** to the right side of your paper and label it as '**S**'

▪ **AND Gate (Carry):**

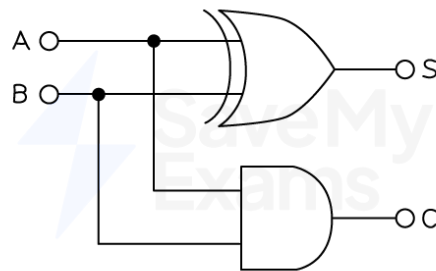- **Draw an AND gate** (typically a D-shaped symbol) above the **XOR gate**. Again, connect the A and B lines to the two inputs of the **AND gate**.
- The output from the **AND gate** is the '**Carry**'. Draw a line from the output of the **AND gate** to the right side of your paper and label it as '**C<sub>out</sub>**'



Copyright © Save My Exams. All Rights Reserved

**Half Adder Logic Gates**

## Full Adders

- **Extends** the half adder to handle the **addition of three bits**
- Has **three inputs**: **A**, **B**, and an input carry (**C<sub>in</sub>**)
- Produces **two outputs**: carry (**C<sub>out</sub>**) and sum (**S**)

A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1



Your notes

0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- To easily reproduce this **Truth Table**, remember:
  - The full adder **adds up three binary inputs** A, B and C
  - So the answer can be **0, 1, 2 or 3**
  - For each row, add up A, B and C and the **write the answer as a 2 bit binary number** in the last 2 columns ( $C_{out}$  and Sum)
  - For example in row 4,  $A=0$ ,  $B=1$  and  $C=1$  -  $0+1+1=2$  which is **10 in binary**, so  $C_{out}$  is **0** and Sum is **1**
  - In the last row,  $A=1$ ,  $B=1$  and  $C=1$ ,  $1+1+1=3$  which is **11 in binary** so  $C_{out}$  is **1** and Sum is **1**

## Operation

- The "Sum" output **provides the XOR** of the inputs A, B, and  $C_{in}$
- The "Carry" output is **TRUE** if at **least two of the inputs** A, B, and  $C_{in}$  are **TRUE**

## Drawing a Full Adder Circuit

- A full adder circuit consists of **three inputs**: A, B, and Carry ( $C_{in}$ ), and **two outputs**: Sum (S) and Carry ( $C_{out}$ )
- It can be designed using **two half adders** and an **OR gate**.
- **Label Inputs**:
  - Start by **drawing three lines** on the left side of your paper or drawing space. Label the top line as 'A', the middle line as 'B', and the bottom line as ' $C_{in}$ '. These represent your inputs
- **First Half Adder**:
  - **Draw a half adder** with A and B as inputs. This consists of an **XOR gate** (for the Sum) and an **AND gate** (for the Carry). Label the output of the XOR gate as '**Sum1**' and the output of the AND gate as '**Carry1**'




Your notes

▪ **Second Half Adder:**

- **Draw a second half adder** underneath the first, using **Sum1** and **C<sub>in</sub>** as inputs. Again, it consists of an **XOR gate** (for the Sum) and an **AND gate** (for the Carry). Label the output of the XOR gate as '**S**' (final Sum) and the output of the **AND gate** as '**Carry2**'

▪ **OR Gate:**

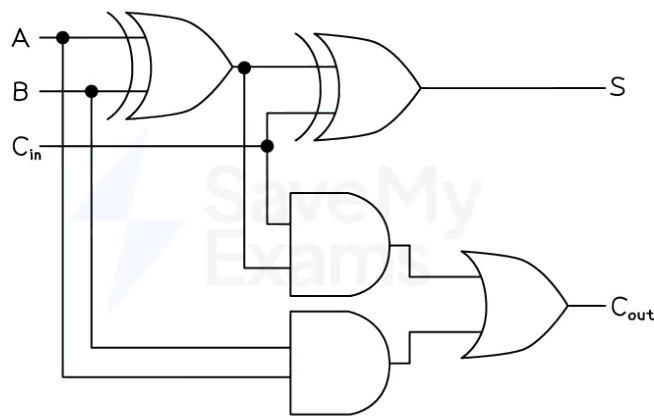- **Draw an OR gate** to the right of the half adders. Connect Carry1 and Carry2 to the inputs of the OR gate. The output of the OR gate is the final Carry (**C<sub>out</sub>**)




Copyright © Save My Exams. All Rights Reserved

**Full Adder Logic Gates**



**Worked Example**

 

Copyright © Save My Exams. All Rights Reserved

Describe how this logic circuit can be adapted to add together two 4-bit binary numbers.

4 marks

**Answer:**

Logic circuit adds together 2 binary digits / half adder

S gives sum, C gives carry

Two half adders can be joined together...

...with an OR gate

to form full adder

4 full adders can be used to add two four bit numbers

Carry out on one joined to carry in on next



Your notes